

$$\# \quad n = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + \text{iron-loss} + \text{cu-loss}}$$

A $P.F. = \frac{kW - \text{active}}{kVA - \text{apparent}}$

$$P_{out} = VI \cos \phi$$

iron loss = constant at any load


$$\text{cu-loss} \sim I^2 \times \text{cu-loss}$$

$$P_{out} = x \times P_{out}$$

$$\therefore h = \frac{x P_{out}}{x P_{out} + x^2 \text{cu-loss} + \text{iron loss}}$$

For max $h = \text{iron loss} = \text{cu-loss}$
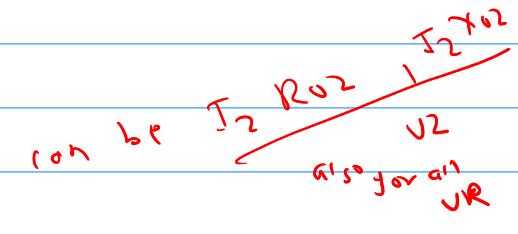
$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2} = k$$



$$V_{reg} \text{ at lag p.f.} = \frac{I_1 R_{o1} \cos \phi_1 + I_1 X_{o1} \sin \phi_1}{V_1} \times 100\%$$

$$V_{reg} \text{ at Unity p.f.} = \frac{I_1 R_{o1}}{V_1} \times 100\%$$

$$V_{reg} \text{ at leading pf} = \frac{I_1 R_{o1} \cos \phi_1 - I_1 X_{o1} \sin \phi_1}{V_1} \times 100\%$$

For max $n = kVA$

$$\text{Load} = \frac{\text{full load } X}{\text{at max } n} = kVA$$

max gauge

iron loss
F-2 cu-loss

A 3Ø transformer

$$3\text{-phase power} \rightarrow P_L = \sqrt{3} V_2 I_2 (\cos \phi)$$

Cu-loss for 3-phase

$$= 3 \times \left(I_{1p} \right)^2 \times R_1 + 3 \times \left(I_{2p} \right)^2 \times R_2$$

primary secondary

$$k = \frac{1}{\sqrt{3}} \frac{V_2}{V_1}$$

① The O.C and S.C test data are given below for a single phase 5kVA, 200V/400V and 50Hz transformer.

O.C test from LV side : 200V 1.25A 150W

S.C test from HV side : 20V 12.5A 175W

Calculate the equivalent ckt parameters referred to primary and secondary ckt and draw the equivalent ckt.


Soln :- Transformer is step-up (LV - HV)


Part - I O.C test

$$V_o = 200V, W_o = 150W, I_o = 1.25A$$

(i) HV side opened

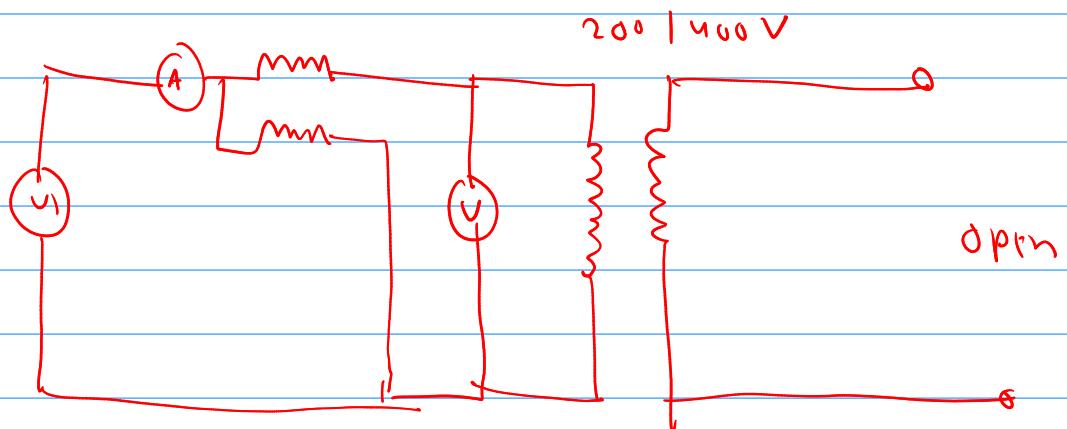(ii) all equipments connected to LV side and supplied by a rated voltage.




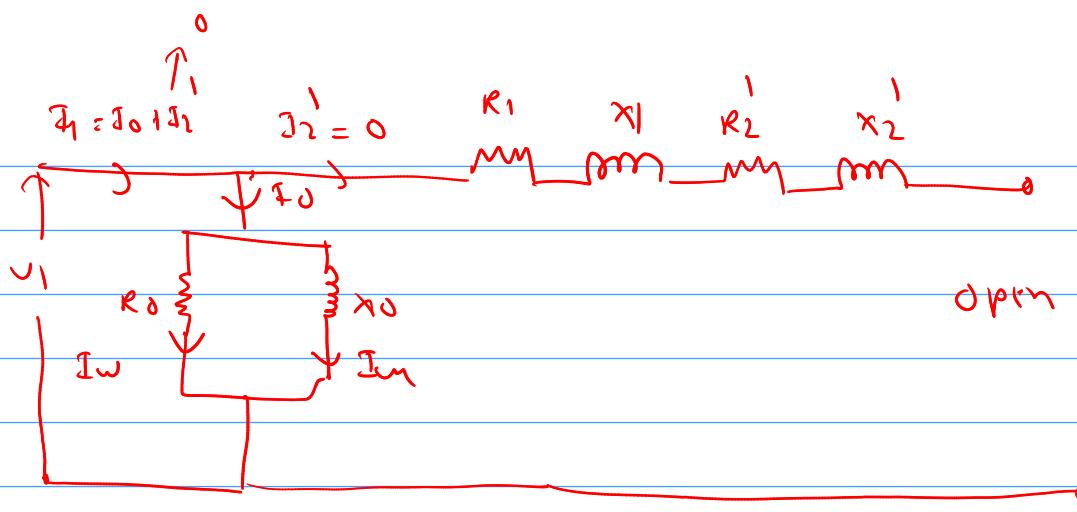

$$I_0 = 1.25 \text{ A}, \quad W_0 = 150 \text{ W}, \quad V_0 = 200 \text{ V} = V_1 \quad \text{Iron loss (iron loss)}$$

/ $W_0 = V_1 I_w$

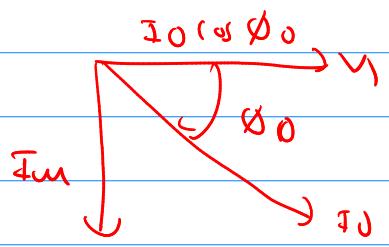Iron loss $W_0 = V_1 \times I_0 \cos \phi_0$



Mg $150 = 200 \times 1.25 \times \cos \phi_0$

$\cos \phi_0$
(magnetic flux)

$$\phi_0 = \cos^{-1} \left(\frac{150}{200 \times 1.25} \right)$$

$$= 53.13^\circ$$

$$I_m = I_0 \sin \phi_0 = 1 \text{ A}$$

$$I_w = I_0 \cos \phi_0 = 0.75 \text{ A}$$

$$R_0 = \frac{V_1}{I_w} = \frac{200}{0.75} = 266.667 \Omega$$

$$X_0 = \frac{V_1}{I_m} = \frac{200}{1} = 200 \Omega$$

$$k = \frac{V_2}{V_1} = \frac{400}{200} = 2$$

$$R_0' = R_0 \times k^2 = 266.667 \times 2^2 = 1066.668 \Omega$$

$$X_0' = X_0 \times k^2 = 200 \times 2^2 = 800 \Omega$$


$$V_{\Phi}' = V_0 \times k = 200 \times 2 = 400 \text{ V}$$

$$I_0' = \frac{1}{k} I_0 = \frac{1}{2} \times 1.25 = 0.625 \text{ A}$$


part - 2 (SIC + Pst)

(i) LV side + SIC

(ii) all component + HV side

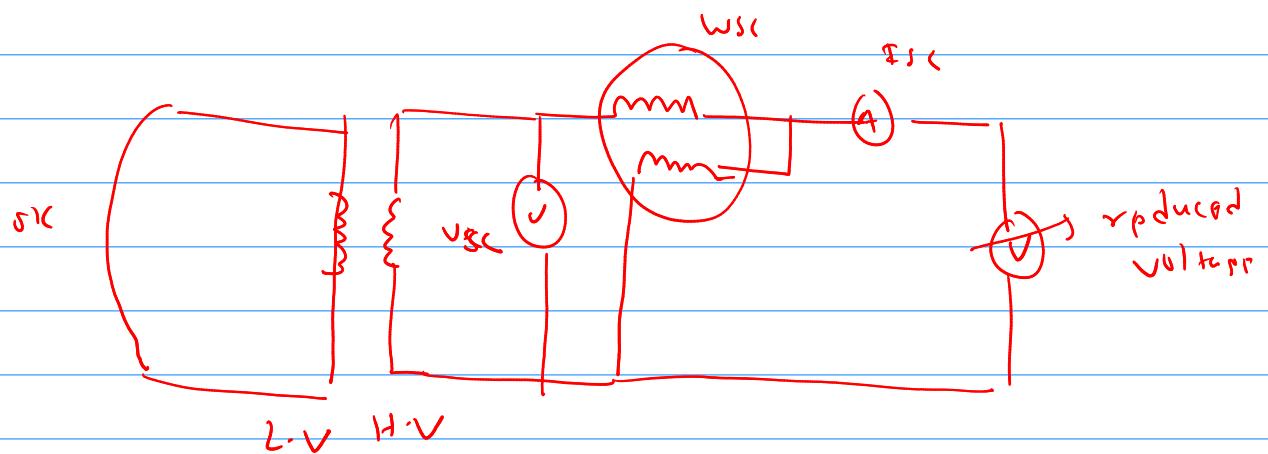

(kt referred to secondary side)

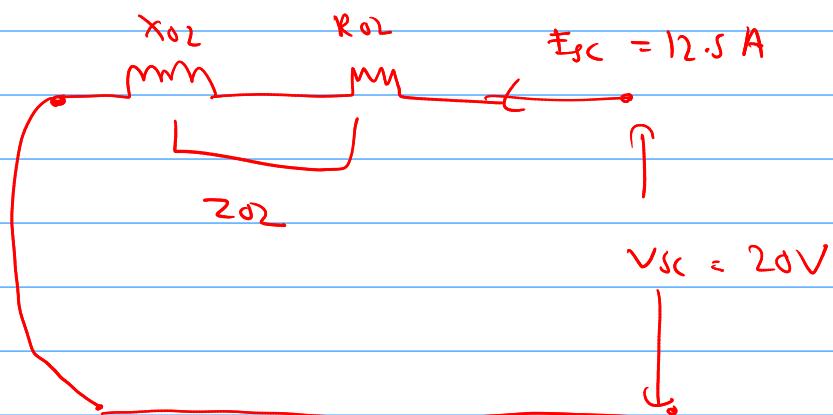

$$W_{sc} = 175 \text{ W} = \text{copper loss}$$

$$V_{SC} = I_{SC} \times Z_{02}$$

$$\text{or } Z_{02} = \frac{V_{SC}}{I_{SC}} = \frac{20}{12.5} = 1.6 \Omega$$

$$W_{SC} = I_{SC}^2 \times R_{02} \quad (\text{cu-loss}) \text{ resistance}$$

$$\text{or } 178 = (12.5)^2 \times R_{02}$$

$$\therefore R_{02} = 1.12 \Omega$$

$$X_{02} = \sqrt{Z_{02}^2 - R_{02}^2} = \sqrt{1.6^2 - 1.12^2} \\ = 1.14 \Omega$$

$$Z_{01} = \frac{Z_{02}}{k^2} = \frac{1.6}{2} = 0.8 \Omega$$

$$R_{01} = \frac{R_{02}}{k^2} = 0.28 \Omega$$

$$X_{01} = \frac{X_{02}}{k^2} = 0.285 \Omega$$

H A 100 kVA / 11 kV / 220 V, 50 Hz single transformer produces the following results.


O.C test : 220V, 45A, 2kW / iron
 S.C test : 500V, 9.03A, 3kW → copper

Soln :


Part I O.C test

$$V_0 = 220V, I_0 = 45A, P_0 = 2kW$$

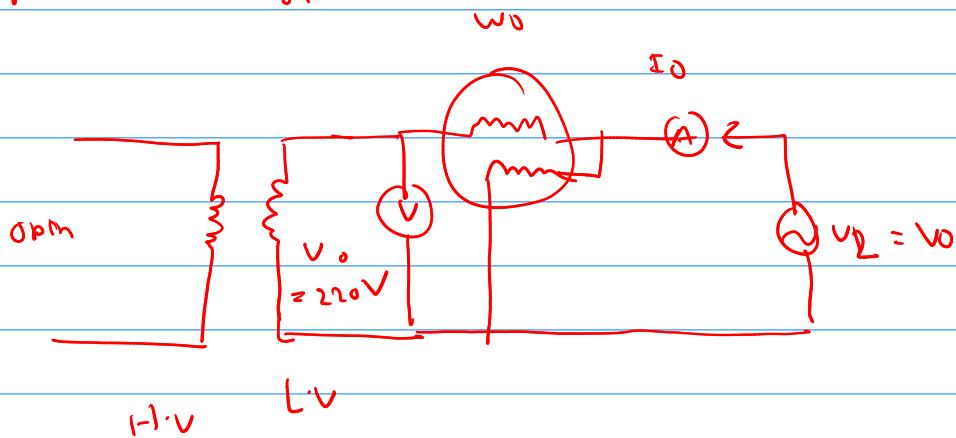- c.i) HV side open
- c.ii) all equipments in LV side supplied by rated voltage.



ref ckt refers to secondary

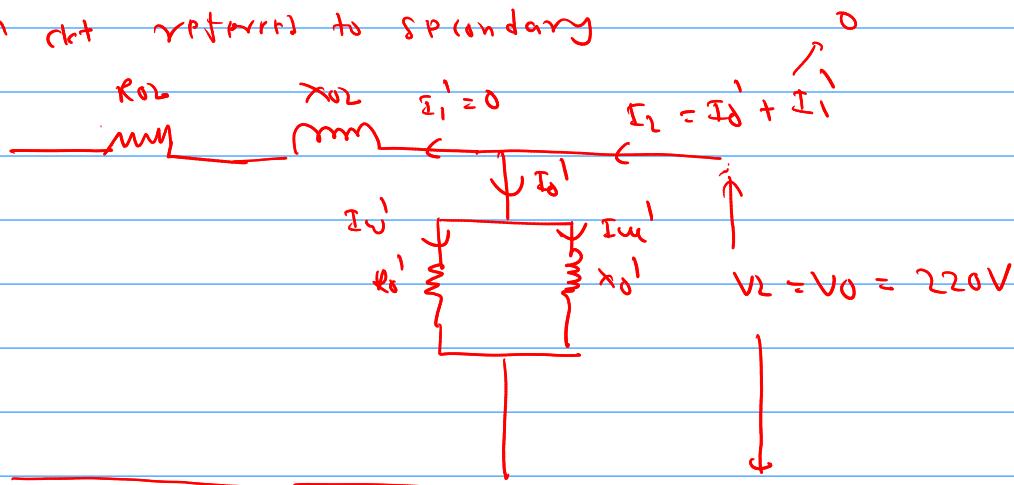

$$V_2 = 220V, \omega_0 = 2 \times 10^3 \text{ rad/s}, I_2 = 45A$$

(give in question)

allow

$$W_0 = 2 \text{ kW} = 2 \times 10^3 \text{ W} \quad (\text{iron})$$


iron loss
 $I\omega^1 = I_d^1 \cos \phi_0^1$

$$W_0 = V_2 \times I\omega^1$$

$$2 \times 10^3 = 220 \times 50^1 \cos \phi_0^1$$

$$(I_2 = I_d^1) \\ \text{ammeter reading}$$
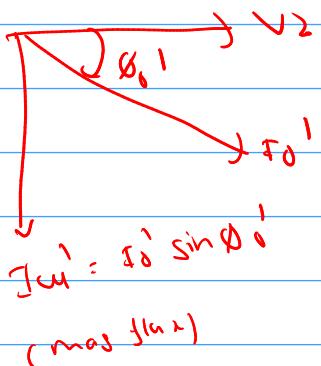
$$\therefore 2 \times 10^3 = 220 \times 45 \cos \phi_0^1$$



$$\text{on } \cos \phi_0^1 = \frac{2 \times 10^3}{220 \times 45}$$

$$\therefore \phi_0^1 = 78.34^\circ$$

$$I\omega^1 = I_d^1 \cos \phi_0^1 = 9.09 \text{ A}$$

$$I\omega^1 = I_d^1 \sin \phi_0^1 = 44.07 \text{ A}$$

$$\text{Then } X_d^1 = \frac{V_2}{I\omega^1} = \frac{220}{44.07} = 4.992 \text{ A}$$

$$R_d^1 = \frac{V_2}{I\omega^1} = \frac{220}{9.09} = 24.20 \text{ A}$$

$$k = \frac{V_2}{V_1} = \frac{220}{11 \times 10^3} = 0.02$$


$$R_0 = \frac{R_d^1}{k^2} = 60500 \Omega \quad \left| \quad X_0 = \frac{X_d^1}{k^2} = 12480 \Omega \right.$$

part - II SIC test


$$V_{SC} = 500 \text{ V}, Z_{SC} = 9.09 \text{ V}, W_{SC} = 3 \text{ kW}$$

① LV is SIC

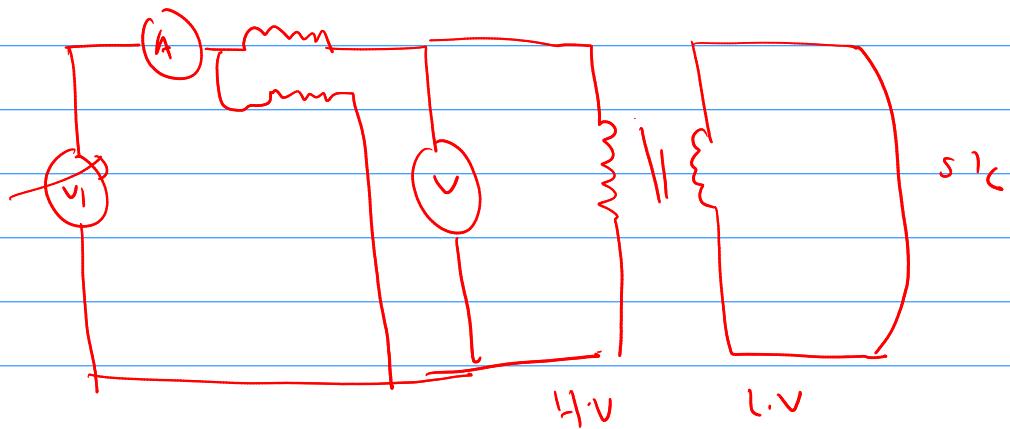② H.V all are connected with reduced rated voltage supply.



Ckt with respect to primary side

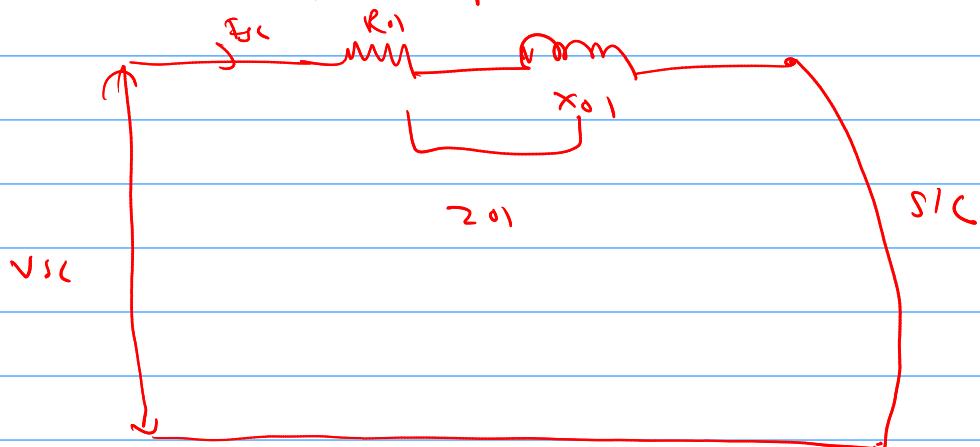

$$Z_{01} = \frac{V_{SC}}{I_{SC}} = \frac{500}{9.09} = 55 \Omega$$

$$W_{SC} = I_{SC}^2 \times R_{01} \quad (\text{cu-loss})$$

$$R_{01} = \frac{V_{SC}}{(I_{SC})^2} = \frac{3 \times 10^3}{(9.01)^2} = 36.307 \Omega$$

$$X_{01} = \sqrt{(Z_{01})^2 - (R_{01})^2} = 41.31 \Omega$$

$$R_{02} = k^2 R_{01} = (0.02)^2 \times 36.307 = 0.014 \Omega$$

$$k = \frac{V_L}{V_I} = 0.02$$

$$X_{02} = k^2 X_{01} = (0.02)^2 \times 41.31 = 0.0165 \Omega$$

$$R_{02} = 0.014 \Omega \quad X_{02} = 0.0165 \Omega$$



Now shift voltage to LV side ↴

capacity



A transformer is rated at 100kVA. At full load its copper loss is 1200W and its iron loss is 760W.

Calculate

- η at full load, unity p.f
- η at half load, 0.8 p.f

Soln:

100 kVA - Transformer

$$\text{Cu-loss} = 1200 \text{ W}$$

$$\text{iron-loss} = 760 \text{ W}$$

$$(i) \eta = \frac{\text{Pout}}{\text{PVA}} \quad \text{Pout} = \text{PVA} \times \text{p.f}$$
$$= 100 \times \text{p.f} \text{ kW}$$

$$\text{at full load } (\alpha = 1) \quad \text{p.f} = 1$$

$$\text{Pout} = 100 \times 1 = 100 \text{ kW}$$

$$\eta = \frac{\text{Pout}}{\alpha \times \text{Pout} + \alpha^2 \times \text{Cu-loss} + \text{iron-loss}}$$

$$= \frac{1 \times 100 \times 10^3}{1 \times 100 \times 10^3 + 1^2 \times 1200 + 760}$$

$$= 0.978 = 97.88\%$$

(ii) at half load ($\alpha = 0.5$) with p.f = 0.8, $\cos \phi = 0.8$

$$P_{out} = V I \cos \phi$$

$$= 100 \text{ kVA} \times 0.8 = 80 \text{ kW}$$

$$\eta - n = \frac{0.5 \times 80}{0.5 \times 80 + (0.5)^2 \times 1.2 + 0.96}$$

$$= 0.9674$$

$$\approx 96.74\%$$

A 1φ 500 kVA transformer working at unity p.f has an efficiency of 90% at half load and iron loss at 2000W. Determine n at full load.

(cos - T)

$$p.f = 1$$

$$n = 90\% = 0.9$$

$$\chi = 0.5$$

$$\text{iron} = 2000 \text{ W} = 2 \text{ kW}$$

$$P_{out} = V I \cos \phi / p.f$$

$$\approx 500 \times 1 = 500 \text{ kW}$$

$$n = \underline{\chi \times P_{out}}$$

$$\chi \times P_{out} + \chi^2 \times (u-1) \chi + \text{iron-loss}$$

$$\text{on } 0.9 = \frac{0.5 \times 500}{0.5 \times 500 + (0.5)^2 \times (u-1) \chi + 2}$$

$$\therefore (u-1) \chi = 103.11 \text{ kW}$$

(ii) $n = ?$

$x = 1$

$$n = \frac{1 \times 500}{1 \times 500 + 1^2 \times 103.111 + 2}$$

$$= 0.8262 = 82.62\% \text{ (full load)}$$

A 20 kVA, 250V / 2500V, 50Hz 1Φ transformer has the following parameters; $R_0 = 600\Omega$, $X_0 = 180\Omega$, $R_{01} = 0.05\Omega$ and $X_{01} = 0.15\Omega$

(i) calculate iron loss

(ii) calculate the primary current at which the n of transformer will be maximum and also calc maximum n .

Soln :-


20 kVA \rightarrow capacity

250 / 2500 V, 50Hz, 1Φ

Step-up ($L.V - H.V$)


$R_0 = 600\Omega$, $X_0 = 180\Omega$ $R_{01} = 0.05\Omega$ $X_{01} = 0.15\Omega$

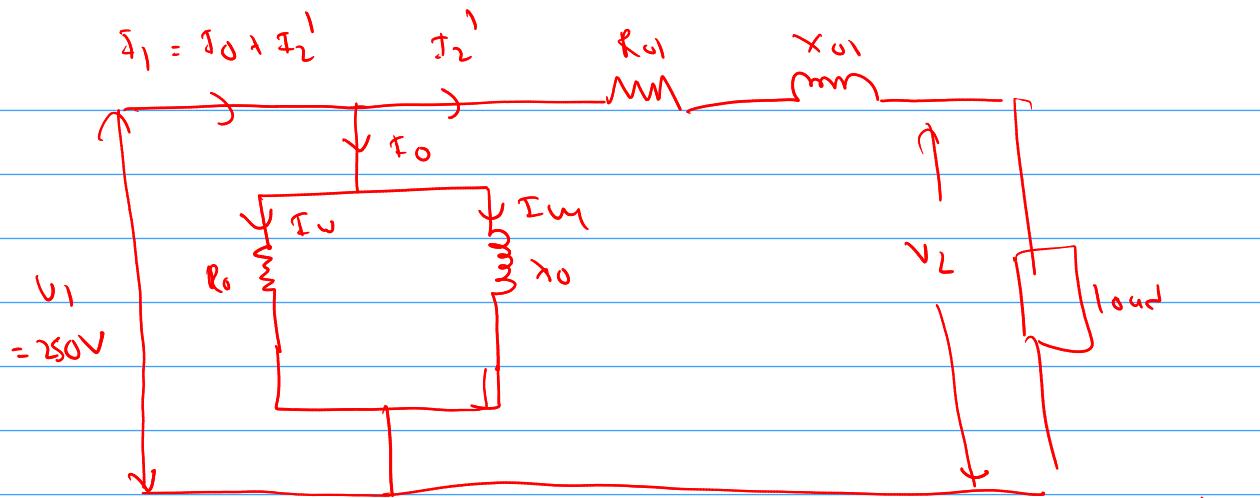drawing each circuit of transformer referred to primary



I_w responsible for iron-loss
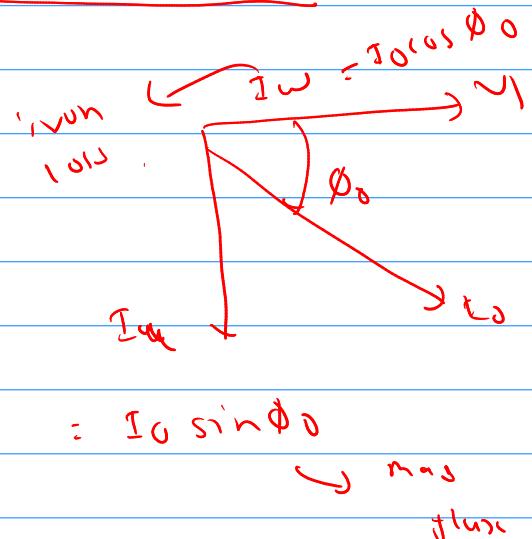
$$\begin{aligned} \text{Iron-loss} &= V_1 I_w \\ &= V_1 I_0 \cos \phi_0 \end{aligned}$$



Hyp,

$$V_1 = I_w \times R_0$$

$$I_w = \frac{V_1}{R_0} = \frac{250}{600} = \frac{5}{12} A$$

$$I_m = \frac{V_1}{X_0} = \frac{250}{180} = \frac{25}{18} A$$

$$\begin{aligned} \text{iron-loss} &= V_1 \times I_w = 250 \times \frac{5}{12} = 104.167 W \\ &= 0.10416 \text{ kW} \end{aligned}$$

For max ϕ

$$\text{iron-loss} = C_u - \text{loss}$$

$$\text{on } 0.10416 = (I_2')^2 \times R_o$$

✓ (u-loss due to heat resistance)

$$\text{or } 0.10416 \times 10^3 = (I_2')^2 \times 0.05$$

$$\therefore I_2' = 45.64 A$$

$$h_{\text{max}} = \frac{P_{\text{out}}}{P_{\text{out}} + 2 \times \text{iron-loss}}$$

(iron = u-loss)

$$h_{\text{max}} = \frac{\sqrt{E} \cos \phi}{\sqrt{E} \cos \phi + 2 \times 0.10416 \text{ kW}}$$

$$= \frac{20 \text{ kVA} \times 1}{20 \text{ kVA} \times 1 + 2 \times 0.10416 \text{ kW}}$$

$$= \frac{20 \text{ kW}}{20 \text{ kW} + 2 \times 0.10416 \text{ kW}}$$

$$= 0.9875 \\ = 98.75 \%$$

- # The no-load current at a transformer is 10 A at a p.f of 0.3 lagging when connected to a 400V, 50Hz power supply. If the primary winding has 500 turns. Calculate
- (i) The magnetizing and working comp of no-load current (I_{w} and I_{m})

(b) iron-loss

(c) max and rms value of ϕ in core

Soln:


$$I_0 = 10 \text{ A} \quad V_1 = 400 \text{ V} \quad N_1 = 300$$

p.d = 0.3 lag (to loss behind V_1) iron loss

$$\cos \phi_0 = \cos 0.3 = 0.3$$

$$\phi_0 = 75.542^\circ$$
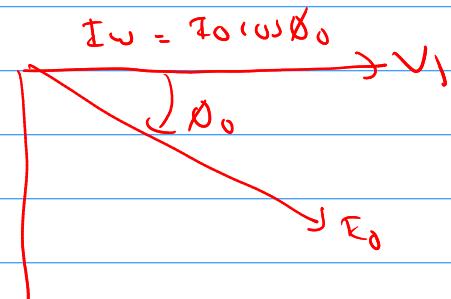
$$I_M = I_0 \sin \phi_0 \\ = 8.537 \text{ A}$$



$$I_M = I_0 \sin \phi_0 \\ \rightarrow \text{flux}$$

$$I_w = I_0 \cos \phi_0 \\ = 10 \times 0.3 \\ = 3 \text{ A}$$

$$\text{iron loss} = V_1 \cdot I_w \\ = 400 \times 3 = 1200 \text{ W}$$

$$E = 4.44 f N_1 \phi_m$$

in (Am)

$$E_1 = V$$

$$V = 4.44 f N_1 \phi_m$$

$$400 = 4.44 \times 50 \times 500 \times \phi_m$$

$$\therefore \phi_m = 3.6036 \times 10^{-3} \text{ wb}$$

$$\Phi_{rms} = \frac{\Phi_m}{\sqrt{2}} = 2.5481 \times 10^{-3} \text{ wb}$$

A 50 kVA, 200 / 2200, 50 Hz 1φ transformer has the following parameters: $R_0 = 600\Omega$, $X_0 = 200\Omega$ referred to primary and $R_{02} = 2\Omega$ and $X_{02} = 4\Omega$ referred to secondary side. Calculate n at transfer when supplying a power of 40 kW to the load with 0.65 pt lagging at rated voltage. Is the transformer over-loaded or under loaded? Calculate the % by which it is over-loaded or under-loaded.

Soln:

50 kVA → capacity

$$200 / 2200V, 50Hz, 1\phi \rightarrow \text{step-up}$$


$$R_0 = 600\Omega, X_0 = 200\Omega$$

$$R_{02} = 2\Omega, X_{02} = 4\Omega$$

$$K = \frac{V_2}{V_1} = \frac{2200}{200} = 11$$

$$R_{01} = \frac{R_{02}}{K^2} = 0.01625\Omega \quad X_{01} = \frac{X_{02}}{K^2} = 0.03305\Omega$$

each ref. referred to primary

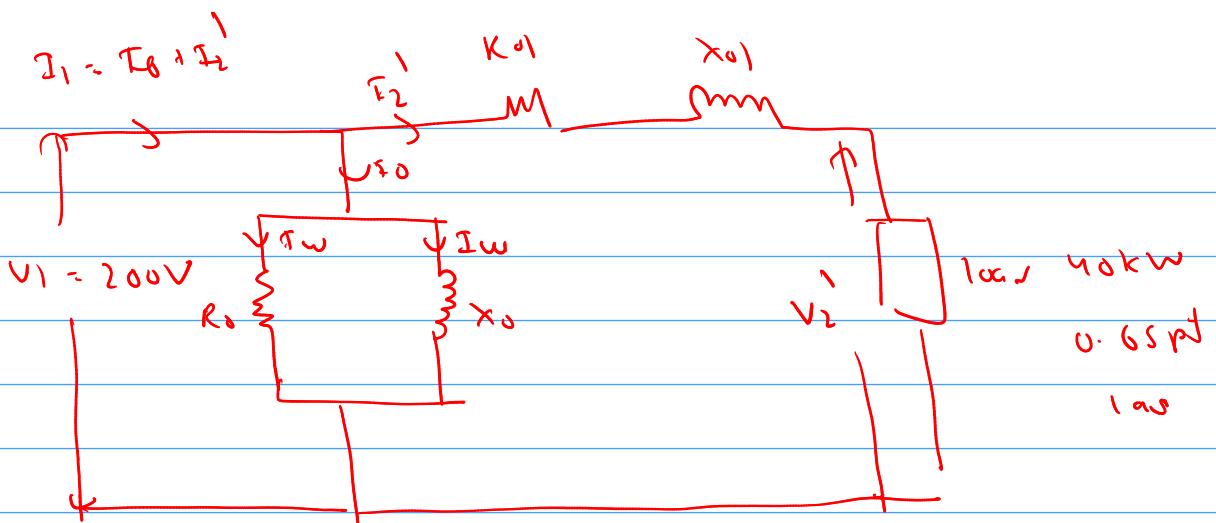

To find if it is overloaded or not

$$\text{Capacity} = 50 \text{ kVA}$$

$$(P+I) = 40 \text{ kW } (0.65 \text{ pf loss})$$

$$\text{P.f} = \frac{\text{kW}}{\text{kVA}}$$

$$\text{Required kVA for load} = \frac{\text{kW}}{\text{P.f}} = \frac{40}{0.65} = 61.53 \text{ kVA}$$

but our capacity is 50 kVA so it is overloaded

$$\% \text{ overload} = \left(\frac{61.53 - 50}{50} \right) \times 100\%$$

$$= 23.06\%$$

$$\eta = \frac{\alpha_{\text{point}}}{\alpha_{\text{point}} + \text{iron} + \text{cu-loss} + \text{core-loss}}$$

$$P_{\text{out}} = V_1 I \cos \phi = 50 \text{ kV} \times 0.65 \\ = 32.5 \text{ kW}$$

$$I_w = \frac{V_1}{R_o} = \frac{200}{600} = \frac{1}{3} \text{ A}$$

$$\text{Iron loss} = V_1 I_w = 200 \times \frac{1}{3} = 66.66 \text{ W}$$

$$(u\text{-loss}) = (I_2')^2 \times R_o$$

Iron loss 0.65

$$u_0 \times 10^3 = V_2' \times I_2' \cos \phi$$

$$u_0 \times 10^3 = 200 \times 0.65 \times \cos \phi \quad I_2'$$

$$\therefore I_2' = 307.69 \text{ A}$$

$$(u\text{-loss}) = (307.69)^2 \times 0.01652 \\ = 1564.023 \text{ W}$$

new logic

$$x = \frac{\text{required kVA}}{\text{given kVA}} = \frac{61.53}{50} = 1.23$$

$$h = \frac{x_{\text{out}}}{x_{\text{out}} + (u\text{-loss} \times x)^2 + \text{iron loss}}$$

$$= \frac{1.23 \times 32.5 \times 10^3}{1.23 \times 35.5 \times 10^3 + (1.23)^2 \times 1564.023 + 66.66} \\ = 0.9425 = 94.25 \%$$

A 200 kVA single phase transformer is in circuit continuous for 8 hrs in a day the load is 160 kw at 0.8 Pf, for 6 hrs, the load is kw at unity power factor & for the remaining period of the day it runs on no load. 80 kW

Given that the full load copper loss = 3.02 kw and iron loss = 1.6 find the all day efficiency of the transformer. [2070]

$$\text{Full load S/p} = 200 \text{ kVA}$$

$$\text{Full load Cu-loss} = 3.02 \text{ kW}$$

$$\text{Full load iron loss} = 1.6 \text{ kW}$$

$$\text{Total energy} = 160 \times 8 + 80 \times 6 + 0 \times 10 \\ = 1760 \text{ kWh}$$

$$\text{iron loss} = 1.6 \text{ kW} \times 24 \\ = 38.4 \text{ kWh}$$

(a) Cu-loss 160 kW 0.8 pf in 8 hrs

hence

$$\text{P.F} = \frac{\text{kW}}{\text{kVA}} \quad 0.8 = \frac{160}{\text{kVA}}$$

$$\text{Required kVA for load} = \frac{160}{0.8} = 200 \text{ kVA}$$

$$W_{Cu} = \left(\frac{200}{200} \right)^2 \times W_{Cu} = 3.02 \text{ kW} \\ = 3.02 \text{ kWh}$$

in 8 hrs

$$W_{Cu} = 3.02 \times 8 = 24.16 \text{ kWh}$$

Cu-loss for load at 80kW at 1 p.f in 6 hr

$$\text{Required kVA for load} = \frac{\text{kW}}{\text{p.f}} = \frac{80}{1} = 80 \text{ kVA}$$

$$W_C = \left(\frac{80}{200} \right)^2 \times W_{Cu}$$

$$= \frac{4}{25} \times 3.02 = 0.4832 \text{ kW}$$

$$W_{Cu} \text{ in } 6 \text{ hr} = 0.4832 \times 6 = 2.899 \text{ kWh}$$

$$\text{IIP energy} = \text{Dip energy} + \text{iron loss} + \\ \{\text{copper loss (8)} + \text{copper loss (6)}\} \text{ hrs}$$

$$= 1760 + 38.4 + 24.16 + 2.899 \text{ kWh} \\ = 1825.4593 \text{ kWh}$$

$$\therefore \text{HdL day} = \frac{\text{Pout}}{\text{Pin}} \times 100\%$$

$$= \frac{1760}{1825.4593} \times 100\%$$

$$= 96.41\%$$

A 25 kVA, 6000 V / 250V single phase transformer has the following parameters $R_1 = 8\Omega$, $X_1 = 15\Omega$, $R_2 = 0.02\Omega$, $X_2 = 0.05\Omega$ calculate the full voltage regulation at power factor.

- @ 0.8 lag
- ⑥ unity
- ⑦ 0.8 lead

Soln :-

$$S = 25 \text{ kVA} \quad V_1 = 6000 \text{ V}$$

$$= 25 \times 10^3 \text{ VA} \quad V_2 = 250 \text{ V}$$

$$R_1 = 8\Omega \quad R_2 = 0.02\Omega \quad T_1 = \frac{S}{V_1} = \frac{25 \times 10^3}{6000}$$

$$X_1 = 15\Omega \quad X_2 = 0.05\Omega$$

$$= 3.78 \text{ A}$$

$$I_2 = \frac{S}{V_2}$$

$$= \frac{25000}{250} = 100 \text{ A}$$

$$k = \frac{V_2}{V_1} = 0.0378$$

Now,

$$R_{01} = R_1 + R_2' \quad S = P$$

$$= 8 + \frac{R_L}{k^2} \quad \left(R_2' = \frac{R_L}{k^2} \right)$$

$$= 8 + \frac{0.02}{(0.0378)^2}$$

$$= 21.97 \Omega$$

$$\begin{aligned}
 R_{01} &= X_1 + X_2 \\
 &= 15 + \frac{0.05}{(0.0371)^2} \\
 &= 49.99 \Omega
 \end{aligned}$$

$$\begin{aligned}
 \cos \phi_1 &= 0.8 \\
 \phi_1 &= 36.86^\circ
 \end{aligned}$$

$$\sin \phi_1 = \frac{3}{5}$$

(a) At 0.8 lag

$$\begin{aligned}
 V_{RIS} &= \frac{I_1 R_{01} \cos \phi_1 + I_1 X_{01} \sin \phi_1 \times 100\%}{V_1} \\
 &= I_1 \left(\frac{R_{01} \cos \phi_1 + X_{01} \sin \phi_1}{V_1} \right) \times 100\% \\
 &\approx 3.78 \left(\frac{21.997 \times 0.8 + 49.99 \times \frac{3}{5}}{6600} \right) \times 100\% \\
 &= 2.72\%
 \end{aligned}$$

(b) At Unity p.f

$$\begin{aligned}
 V_{RIS} &= \frac{I_1 R_{01} \times 100\%}{V_1} = \frac{3.78 \times 21.997}{6600} \\
 &= 1.25\%
 \end{aligned}$$

(c) at 0.8 pf lag

$$V_{RIS} = I_1 \left(\frac{R_{01} \cos \phi_1 - X_{01} \sin \phi_1}{V_1} \right) \times 100\%$$

$$\eta_{eff} = 3.78 \left(\frac{21.997 \times 0.8 - 19.99 \times \frac{3}{5}}{660} \right) \times 100\% \\ = -0.71\%$$

- # Q4 The efficiency of a 1000 KVA, 110/220V, 50 Hz single phase transformer is 98.5% at half load at 0.8 p.f. leading & 98.8% full load unity P.F. Determine
 (i) iron loss
 (ii) full load copper loss
 (iii) Maximum efficiency at unity P.F.

Soln :-

$$V_1 = 110V \quad V_2 = 220V \quad f = 50Hz$$

$$\eta = \frac{\text{ac power}}{\text{ac power} + \text{ac } w_c + w_i}$$

(i) For half load ($\cos \phi = 0.8$) $\text{p.f.} = 0.8$ (leading) $\eta = 98.5\%$

$$\frac{98.5}{100} = \frac{0.5 \times V_2 I_2 \cos \phi}{0.5 \times V_2 I_2 \cos \phi + (0.5)^2 \times w_c + w_i}$$

$$0.985 = \frac{0.5 \times 1000 \times 0.5}{0.5 \times 1000 \times 0.5 + 0.5^2 w_c + w_i}$$

$$0.985 = \frac{250}{250 + 0.25 w_c + w_i}$$

$$\text{or } 246.25 + 0.24625 w_c + 0.985 w_i = 250$$

$$\therefore 0.24625 w_c + 0.985 w_i = 3.75 \quad \text{---(i)}$$

at p.t \rightarrow (i) full load, $n = 98.8\%$

$$0.988 = \frac{1000 \times 1}{1000 \times 1 + w_c + w_i}$$

$$\text{or } 1000 + w_c + w_i = 1012.14$$

$$\therefore w_c + w_i = 12.145 \quad \text{---(ii)}$$

Solve (i) and (ii)

$$w_c = 11.117 \text{ kW}$$

$$w_i = 1.02 \text{ kW}$$

$$(\text{load} = \text{full load} \times \sqrt{\frac{\text{iron}}{(\eta)} \text{ loss}})$$

For η mark

$$\text{iron} = (\eta - \text{loss})$$

$$1.02 = x^2 \times 11.117$$

$$\therefore x =$$

$$\sqrt{\frac{1.02}{11.117}} = 0.30$$

$$\text{iron loss} = (\eta - \text{loss})$$

$$\eta = \frac{x \cdot P_{\text{out}}}{x \cdot P_{\text{out}} + 2xw_i} = \frac{0.3 \times 1000 \times 1}{0.3 \times 1000 \times 1 + 2 \times 1.02}$$

$$= 99\%$$

↑

↳ *mark* $\eta = \frac{P_{\text{out}}}{P_{\text{out}} + 2xw_i}$

mark η
some η
at 60% η

A 600 kVA, 1Ø transformer has η at 92% both at full load and half load at unity p.f. Determine η at 60% at full load at 0.8 p.f lag.

Soln :-

$$\eta = \frac{2 \times \text{kVA} \times \cos \phi}{2 \times \text{kVA} \times \cos \phi + W_i + \alpha^2 W_C} \times 100 \%$$

At F.L Unit p.f

$$\eta = \frac{1 \times 600 \times 1}{1 \times 600 \times 1 + W_i + W_C} \times 100$$

$$\therefore W_i + W_C = 52.174 \text{ kW} \quad \text{---(i)}$$

At half load p.f

$$\eta = \frac{0.5 \times 600 \times 1}{0.5 \times 600 \times 1 + W_i + (0.5)^2 \times W_C} \times 100$$

$$\text{or } W_i + 0.25 W_C = 26.087 \text{ kW}$$

$$\text{So, } W_i = 17.39 \text{ kW}, \quad W_C = 34.78 \text{ kW}$$

$$\text{Also } 60\% \text{ FL, } 0.8 \text{ p.f} \quad \alpha = 0.6$$



$$\begin{aligned} \eta &= \frac{0.6 \times 600 \times 0.8}{0.6 \times 600 \times 0.8 + 17.39 + 0.6^2 \times 34.78} \times 100 \% \\ &= 90.59 \% \end{aligned}$$

3 ϕ numerically
given voltage is line
voltage

A 132 kV / 11 kV star / delta, 3 ϕ transformer has balanced star connected 3-phase load of 4 MW at p.f. of 0.8 lag per phase. The primary winding has resistance and leakage reactance of 10Ω and 30Ω respectively. The secondary winding has resistance and leakage reactance of 0.02Ω and 0.06Ω respectively. Given that iron loss at the transformer is 20 kW

Calculate :-

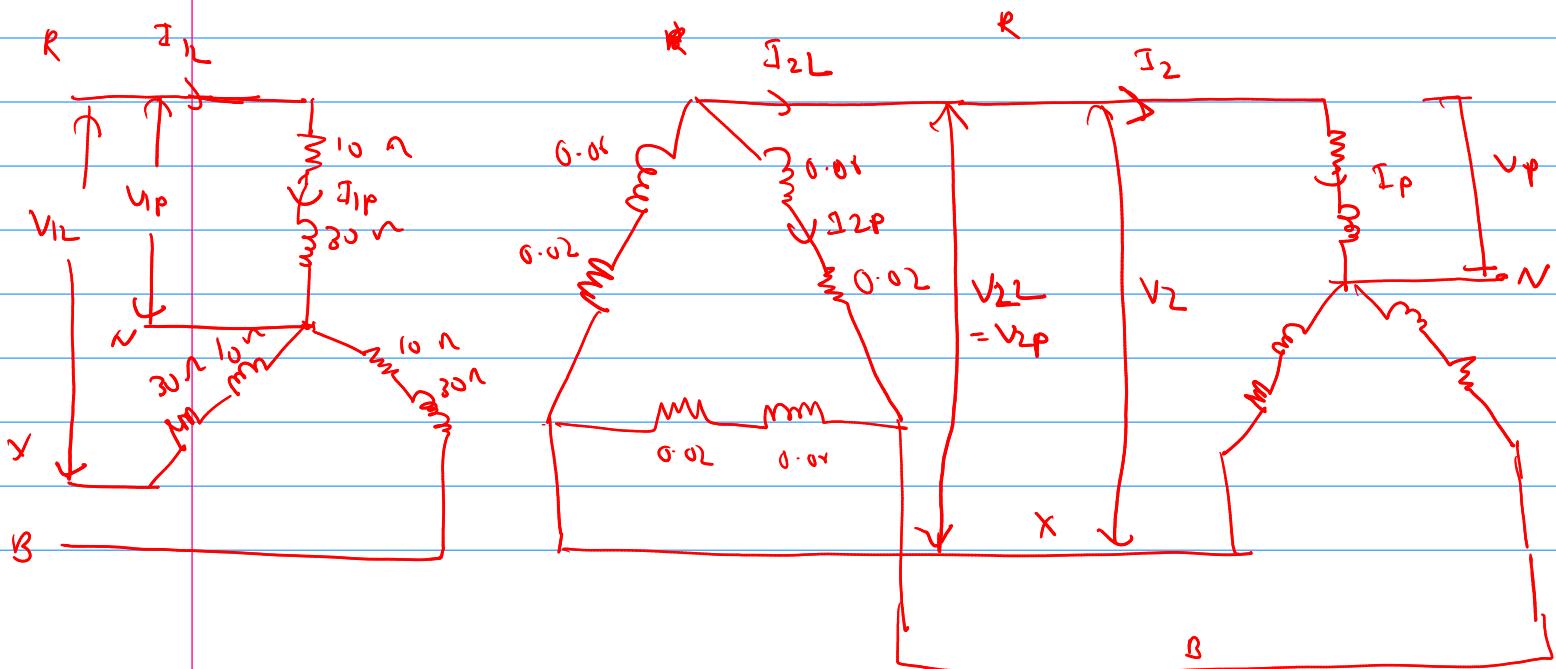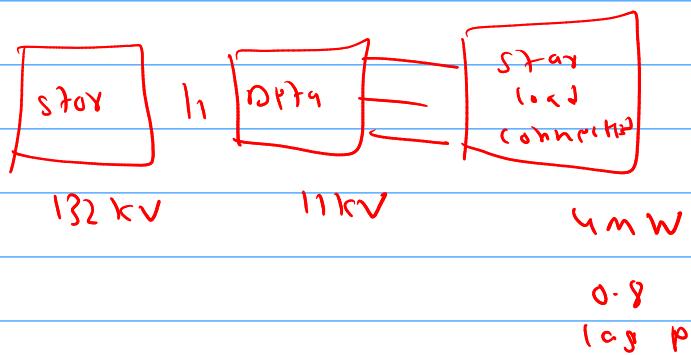- ① Secondary phase and line current (I_{2p} , I_{2L})
- ② Primary line current (I_{1L})
- (iii) efficiency of the transformer. (%)



N.W.	Star	Delta	Load
$V_{1L} = 132 \text{ kV}$	$V_{2L} = 11 \text{ kV}$ $V_{2P} = V_{2L} = 11 \text{ kV}$	$I_{2P} = \frac{I_{2L}}{\sqrt{3}}$	$P_f = 0.8 \text{ lag}$ $P = 4 \text{ MW}$ $V_L = V_{2L} = 11 \text{ kV}$ $P_L = \sqrt{3} V_L I_2 \cos \phi$ (3% power)
$V_{1P} = \frac{V_{1L}}{\sqrt{3}}$ = $\frac{132}{\sqrt{3}}$ = $44\sqrt{3} \text{ kV}$			

$$P_L = V_L I_2 \cos \phi$$

$$6 \times 10^6 \text{ W} = \sqrt{3} \times 11 \times 10^3 \times I_2 \times 0.8$$

$$\therefore I_2 = 262.431 \text{ A}$$

$$\therefore I_L = I_{2L}$$

$$\boxed{\therefore I_{2L} = 262.431 \text{ A}}$$

$$\boxed{I_{2P} = \frac{I_{2L}}{\sqrt{3}} = \frac{262.431}{\sqrt{3}} = 181.51 \text{ A}}$$

N.W.,

$\omega^2 \propto \omega$

$$\frac{v_2}{v_1} = \frac{V_2}{V_1} = \frac{I_1}{I_2}$$

$$01 \quad \frac{V_{2P}}{V_{1P}} = \frac{I_{1P}}{I_{2P}}$$

$$01 \quad \frac{|I|}{44\sqrt{3}} = \frac{I_{1P}}{151.5}$$

$$\therefore I_{1P} = 21.8685 \text{ A}$$

$$\therefore I_{1P} = I_L$$

$$\therefore \boxed{I_{1L} = 21.8685 \text{ A}}$$

$$\eta = \frac{P_{out}}{P_{out} + \cancel{R_{iron}} + (u\text{-loss})}$$

$$iron\text{-loss} = 20 \text{ kW} \quad (\text{const})$$

$$cu\text{-loss} = I^2 R$$

for 3-phase

$$cu\text{-loss} = 3 \times (I_{1P})^2 \times R_1 + 3 \times (I_{2P})^2 \times R_2$$

$$\begin{aligned} &= 3 \times (21.8685)^2 \times 10 + 3 \times (151.5)^2 \times 0.02 \\ &\approx 15724.2557 \text{ W} \\ &\approx 15.72 \text{ kW} \end{aligned}$$

$$P_{out} = 4mW = 4 \times 10^6 \text{ W} = 4 \times 10^3 \text{ kW}$$


$$\eta = \frac{u \times 10^3}{u \times 10^3 + 20 + 15.72425} = 0.99114$$

$$= 99.114\%$$

V_{11} \rightarrow line voltage

An 11kV / 380V delta / star 3Ø transformer has balanced star connected 3Ø load of 40kW at p.f at 0.8 lagging per phase. calculate the primary line current , if the transformer has iron loss of 1.0 kW , calculate the approximate efficiency of the transformer . Given that primary winding resistance and leakage reactance are 25Ω per phase and 40Ω per phase respectively . Secondary winding resistance and leakage reactance are 0.01Ω per phase and 0.02Ω per phase respectively .

SOLN :-

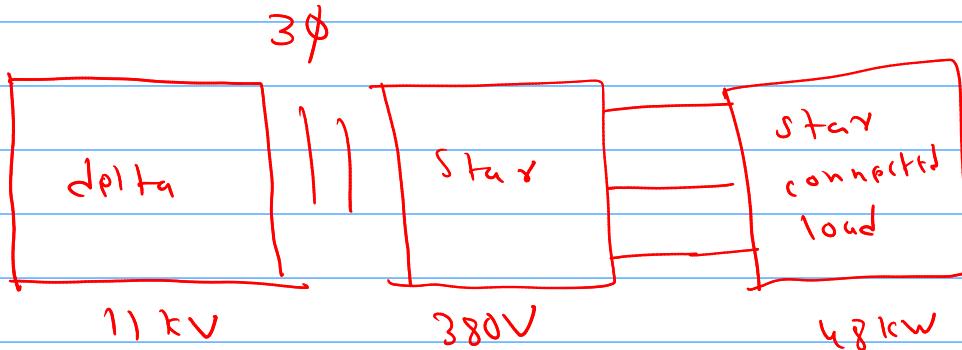

0.8 lagging

$$\eta = \frac{P_{out}}{P_{out} + \text{iron} + \text{cu-loss}}$$


per phase

$$I_{21} = ?$$

$$\text{iron loss} = 1 \text{ kW}$$

$$(\text{iron loss}) = 3(I_{1p})^2 R_1 + 3(I_{2p})^2 R_2$$

$$P_{\text{out}} = \sqrt{3} V_2 I_2 \cos \phi$$

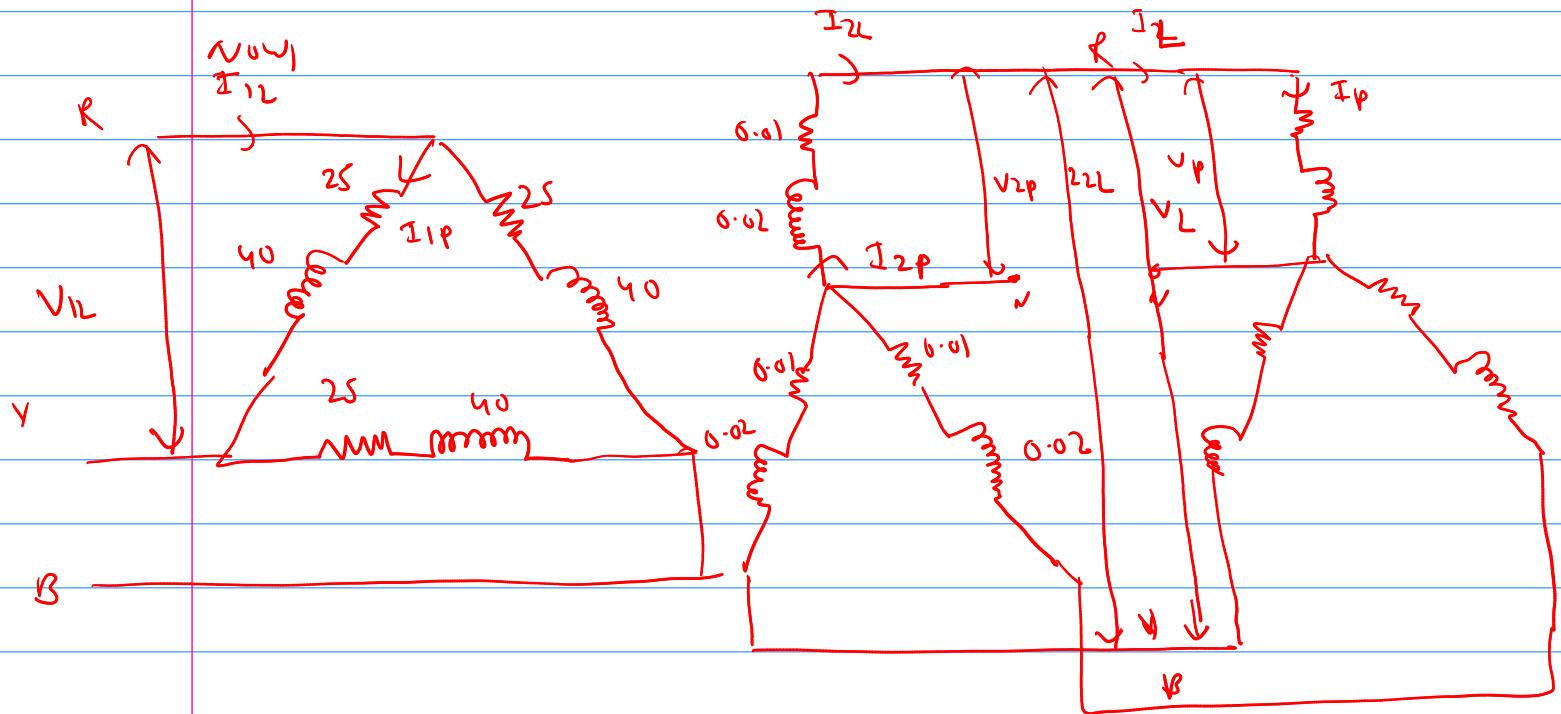

NBB_1

$$V_{1p} = V_{1L} = 11 \text{ kV}$$

$$I_{1p} = \frac{I_{1L}}{\sqrt{3}}$$

$$V_{2p} = \frac{V_{2L}}{\sqrt{3}}$$

$$V_{2L} = 380 \text{ V} = V_L$$

$$V_{2p} = \frac{V_{2L}}{\sqrt{3}} = \frac{380}{\sqrt{3}} = 219.39 \text{ V} = V_p$$

$$I_{2L} = I_L = I_{2p}$$

NRW,

load 40kW 0.8 lag ppr phase

$$P_2 = 40 \text{ kW}$$

$$\text{or } P_2 = V \sqrt{3} V_L I_2 \cos \phi$$

$$\text{or } 40 \times 10^3 = \sqrt{3} \times 380 \times 0.8 \times I_L$$

$$\therefore I_L = 75.96 \text{ A}$$

$$\boxed{I_L = I_{2L} = I_{rp} = 75.96 \text{ A}}$$

NRW

$$\frac{N_2}{N_1} = \frac{V_L}{V_1} = \frac{I_1}{I_2}$$

$$\frac{V_{2L}}{V_{12}} = \frac{I_{1L}}{I_{2L}}$$

$$\text{or } \frac{380}{11} = \frac{I_{1L}}{75.96}$$

$$\therefore \boxed{I_{1L} = 2.624 \text{ A}}$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{out}} + \text{Iron loss} + \text{Cu-loss}}$$

$$\text{Iron-loss} = I_0^3 \text{ W}$$

$$\text{Cu-loss} = 3 \times (I_{1p})^2 \times R_1 + 3 \times (I_{rp})^2 \times R_2$$

$$\text{cu-loss} = 3 \cdot \left(\frac{2.124}{\sqrt{3}} \right)^2 \times 25 + 3(75.96) \times 0.01$$

$$= 345.2941 \text{ W}$$

$$n = \frac{40 \times 10^3}{40 \times 10^3 + 1000 + 345.294}$$

$$= 0.96746$$

$$= 96.746\%$$

Note \rightarrow if primaries with all resistances not same
and secondary

$$\text{cu-loss} = (I_{1p})^2 (R_{11} + R_{12} + R_{13}) + (I_{2p})^2 (R_{21} + R_{22} + R_{23})$$

mathi ko mali all resistance in 3 δ star and delta
sum su

$$3 \times (I_{1p})^2 \times R_1 \quad r_3 \times (I_{2p})^2 \times R_2$$

A 50kVA, 6000 / 400V Y/Y 3 δ 50Hz transformer
has an iron loss of 1600W - The maximum
efficiency occurs at $\frac{3}{4}$ full load. Find the
efficiency of the
transformer at

- (i) full-load and 0.8 pf
(ii) half-load and unity p.f

Soln :-

For max efficiency

$$C_u\text{-loss} = \text{iron-loss}$$

Max η occurs at $\frac{3}{4}$ full load

$$\text{Full load, } C_u\text{-loss} = 3(I_{1p})^2 R_1 + 3(I_{2p})^2 R_2$$

$$C_u\text{-loss at } \frac{3}{4}\text{-load} = \frac{2}{3} \times C_u\text{-loss at full load}$$

For n to be max

$$\text{Iron loss} = x^2 \times C_u\text{-loss}$$

$$x \rightarrow \frac{3}{4}$$

$$\text{Iron loss} = \left(\frac{3}{4}\right)^2 \times C_u\text{-loss}$$

$$\text{or, } 1600 = \left(\frac{3}{4}\right)^2 \times C_u\text{-loss}$$

$$\therefore C_u\text{-loss} = 2844.44 \text{ W}$$

$$\text{Iron loss} = 1600 \text{ W}$$

(i) at full load ($\alpha = 1$) $\rho.f = 0.8$

$$\eta = \frac{\alpha \times P_{out}}{\alpha \times P_{out} + I^2 \times Cu\text{-loss} + Tron\text{ loss}}$$

$$Cu\text{-loss} = 2844.44 \text{ kW}$$

$$Tron\text{ loss} = 1600 \text{ W}$$

$$\begin{aligned} P_{out} &= \sqrt{3} V_L I_L \cos \phi \quad (\text{3-phase}) \\ &= 120 \text{ kVA} \times 0.8 \rightarrow \rho.f \\ &= 96 \text{ kW} \end{aligned}$$

$$\begin{aligned} \eta &= \frac{1 \times 96 \times 10^3}{1 \times 96 \times 10^3 + 1^2 \times 2844.44 + 1000} \\ &= 0.9557 = 95.57\% \end{aligned}$$

(ii) half load ($\alpha = 0.5$) and $\rho.f = 1$

$$\begin{aligned} P_{out} &= \sqrt{3} V_L I_L \cos \phi \\ &\approx 120 \text{ kW} \end{aligned}$$

$$\begin{aligned} \eta &= \frac{0.5 \times 120}{0.5 \times 120 \times 10^3 + 0.5^2 \times 2844.44 + 1600} \\ &= 0.9629 \\ &= 96.29\% \end{aligned}$$